

ELEC5803 HLS Exam Study

Step-by-Step Solution to Question 4

Course-slide basis

This solution follows the **sensitive path algorithm**, **fault coverage**, and **test coverage** definitions from Slides/ELEC5803_Slides10_Testability and Dependability_AA2.pdf.

1. Interpreting the circuit

From the gate symbols in the exam figure, the labeled nodes are interpreted as

$$\begin{aligned}D &= A \cdot B, \\E &= B + C, \\F &= B \cdot C, \\H &= E \cdot F, \\G &= D + H.\end{aligned}$$

So the circuit can be redrawn as:

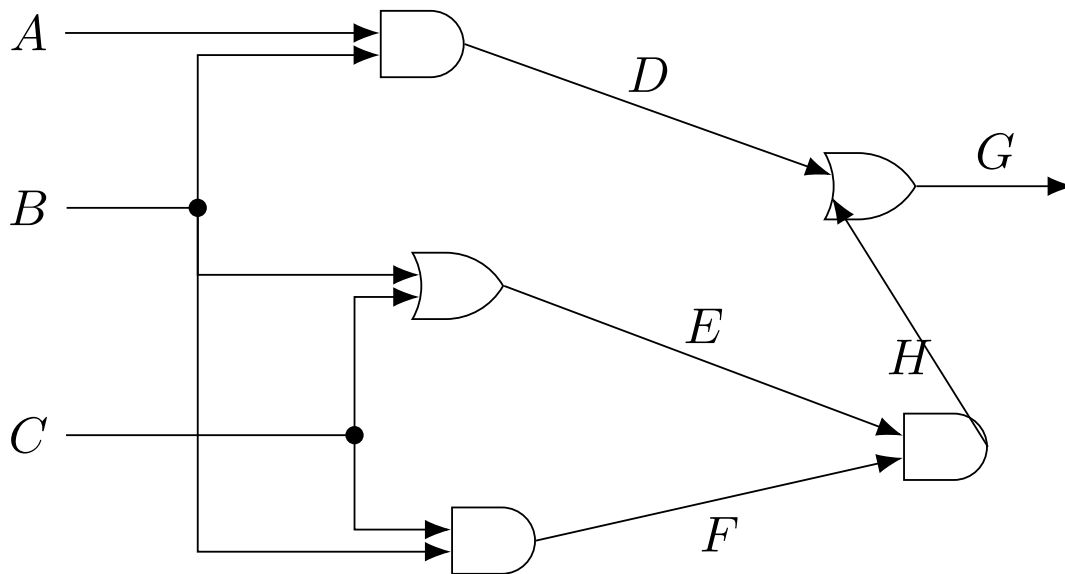


Figure 1: Native-LaTeX redraw of the Q4 circuit.

2. Stuck-at fault list

The question asks about points (A, B, C, D, E, F, G, H) . Under the single stuck-at fault model, each point may be stuck at 0 or stuck at 1.

Therefore the full fault list has

$$8 \times 2 = 16$$

faults:

$$\{A/0, A/1, B/0, B/1, C/0, C/1, D/0, D/1, E/0, E/1, F/0, F/1, G/0, G/1, H/0, H/1\}.$$

3. Part (a): minimum test pattern set using the sensitive path algorithm

3.1 Sensitive path method from the slides

The slides summarize the method as:

1. select a fault,
2. force the faulty node to the opposite logic value in the fault-free circuit,
3. sensitize a path from that node to an observable output,
4. check consistency,
5. use one test to cover as many faults as possible.

3.2 Derive representative tests

Test 1: detect $A/0$ To detect $A/0$, the fault-free value at A must be 1, so set

$$A = 1.$$

Since A is only observable through

$$A \rightarrow D \rightarrow G,$$

we must make

$$B = 1$$

so that $D = A \cdot B$ depends on A .

Also, the other OR input must be 0 so that D is visible at G :

$$H = 0.$$

One simple choice is

$$C = 0 \Rightarrow F = B \cdot C = 0 \Rightarrow H = E \cdot F = 0.$$

Hence a valid test is

$$\boxed{110/10}$$

where the fault-free output is $(G, H) = (1, 0)$.

Test 2: detect $A/1$ To detect $A/1$, force the fault-free value

$$A = 0.$$

Again choose

$$B = 1$$

to let D depend on A , and choose

$$C = 0$$

to force $H = 0$ and sensitize the path to G .

So another valid test is

$$\boxed{010/00}.$$

Test 3: detect $E/0$ To detect $E/0$, the fault-free value at E must be 1:

$$E = B + C = 1.$$

To observe E through

$$E \rightarrow H \rightarrow (H, G),$$

the other input of the AND gate must be 1:

$$F = 1.$$

Since

$$F = B \cdot C,$$

this requires

$$B = 1, \quad C = 1.$$

Using

$$A = 0$$

avoids unnecessary masking through D .

Thus a valid test is

$$\boxed{011/11}.$$

Test 4: detect $B/1$ To detect $B/1$, the fault-free value at B must be 0:

$$B = 0.$$

Choose

$$A = 0, \quad C = 1.$$

Then in the fault-free circuit:

$$D = 0, \quad E = 1, \quad F = 0, \quad H = 0, \quad G = 0.$$

If B is stuck at 1:

$$E = 1, \quad F = 1, \quad H = 1, \quad G = 1.$$

So the fault is observable at both outputs.

Hence a valid test is

$$\boxed{001/00}.$$

3.3 Minimum test set

Collecting the four tests above:

$$\boxed{T = \{001/00, 010/00, 011/11, 110/10\}}.$$

This set detects all detectable faults of the circuit.

3.4 Faults covered by each test

Test vector	Faults detected
001/00	$B/1, D/1, F/1, G/1, H/1$
010/00	$A/1, C/1, D/1, F/1, G/1, H/1$
011/11	$B/0, C/0, E/0, F/0, G/0, H/0$
110/10	$A/0, B/0, C/1, D/0, F/1, G/0, H/1$

3.5 Untestable fault

The only undetectable fault is

$$\boxed{E/1}.$$

Reason: To detect $E/1$, the fault-free circuit must have

$$E = 0.$$

But to propagate E through the AND gate to H , we must also have

$$F = 1.$$

Since

$$F = B \cdot C,$$

$F = 1$ implies

$$B = 1, \quad C = 1.$$

However then

$$E = B + C = 1,$$

which contradicts the requirement that the fault-free value of E be 0.

Therefore no sensitive path test exists for $E/1$.

4. Part (b): fault coverage and test coverage

From the slides:

$$FC = \frac{N_{\text{det}}}{N} \times 100\%, \quad TC = \frac{N_{\text{det}}}{\hat{N}} \times 100\%$$

where:

- N = total number of faults,
- N_{det} = number of detected faults,
- $\hat{N}$ = number of detectable faults.

4.1 Count the faults

$$N = 16.$$

Since only $E/1$ is undetectable,

$$\hat{N} = 15.$$

Our test set detects all detectable faults, so

$$N_{\text{det}} = 15.$$

4.2 Fault coverage

$$FC = \frac{15}{16} \times 100\% = 93.75\%.$$

4.3 Test coverage

$$TC = \frac{15}{15} \times 100\% = 100\%.$$

4.4 Final answer for part (b)

$$FC = 93.75\%, \quad TC = 100\%.$$

5. Part (c): observability and testability of each point

Point	Observability / testability	Discussion
<i>A</i>	Good controllability, medium observability	As a primary input, <i>A</i> is easy to set to 0 or 1. It is observable only through <i>D</i> and then <i>G</i> , so the path must be sensitized by forcing $B = 1$ and $H = 0$. Both $A/0$ and $A/1$ are detectable.
<i>B</i>	Good controllability, good observability	<i>B</i> fans out to <i>D</i> , <i>E</i> , and <i>F</i> , so changes at <i>B</i> can affect both <i>H</i> and <i>G</i> . This gives several detection opportunities, and both stuck-at faults are detectable.
<i>C</i>	Good controllability, medium observability	<i>C</i> affects <i>E</i> and <i>F</i> , then reaches outputs through <i>H</i> and <i>G</i> . It is less directly observable than <i>B</i> , but both $C/0$ and $C/1$ are still detectable.
<i>D</i>	Good observability when $H = 0$	<i>D</i> reaches the output only through the final OR gate, so to observe <i>D</i> we must force the other OR input to 0. Hence <i>D</i> is reasonably testable, but only after sensitization.
<i>E</i>	Poor observability, poorest testability	<i>E</i> is observable only through $H = E \cdot F$, so we need $F = 1$ to make <i>E</i> visible. This allows testing $E/0$, but makes $E/1$ impossible to test. Thus <i>E</i> is the weakest point in the circuit.
<i>F</i>	Good observability when $E = 1$	<i>F</i> can be observed at <i>H</i> and then at <i>G</i> , provided the other AND input is set to 1. Both stuck-at faults are detectable.
<i>G</i>	Highest observability	<i>G</i> is a primary output, so any fault effect reaching <i>G</i> is directly visible. Both $G/0$ and $G/1$ are easy to test.
<i>H</i>	Very high observability	<i>H</i> is directly labeled as an observable node and also feeds <i>G</i> . This makes it one of the easiest internal nodes to observe and test.

6. Final exam-style answers

(a)

Using the sensitive path algorithm, a minimum test set is

$$T = \{001/00, 010/00, 011/11, 110/10\}.$$

(b)

The set detects 15 of the 16 stuck-at faults. Since only $E/1$ is undetectable:

$$\boxed{FC = 93.75\%, \quad TC = 100\%.$$

(c)

Among all points, E has the poorest observability and testability because one of its stuck-at faults ($E/1$) is untestable. Points G and H have the best observability because they are directly observable outputs / output-near nodes.